
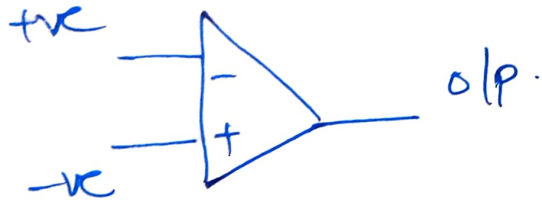


Design of 2 staged OPAMP

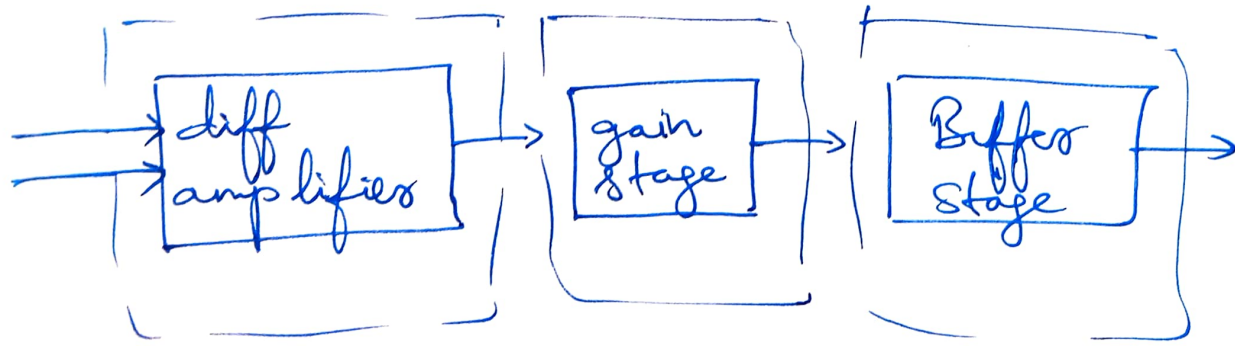


differential i/p
differential amp.



Differential Amplifiers:
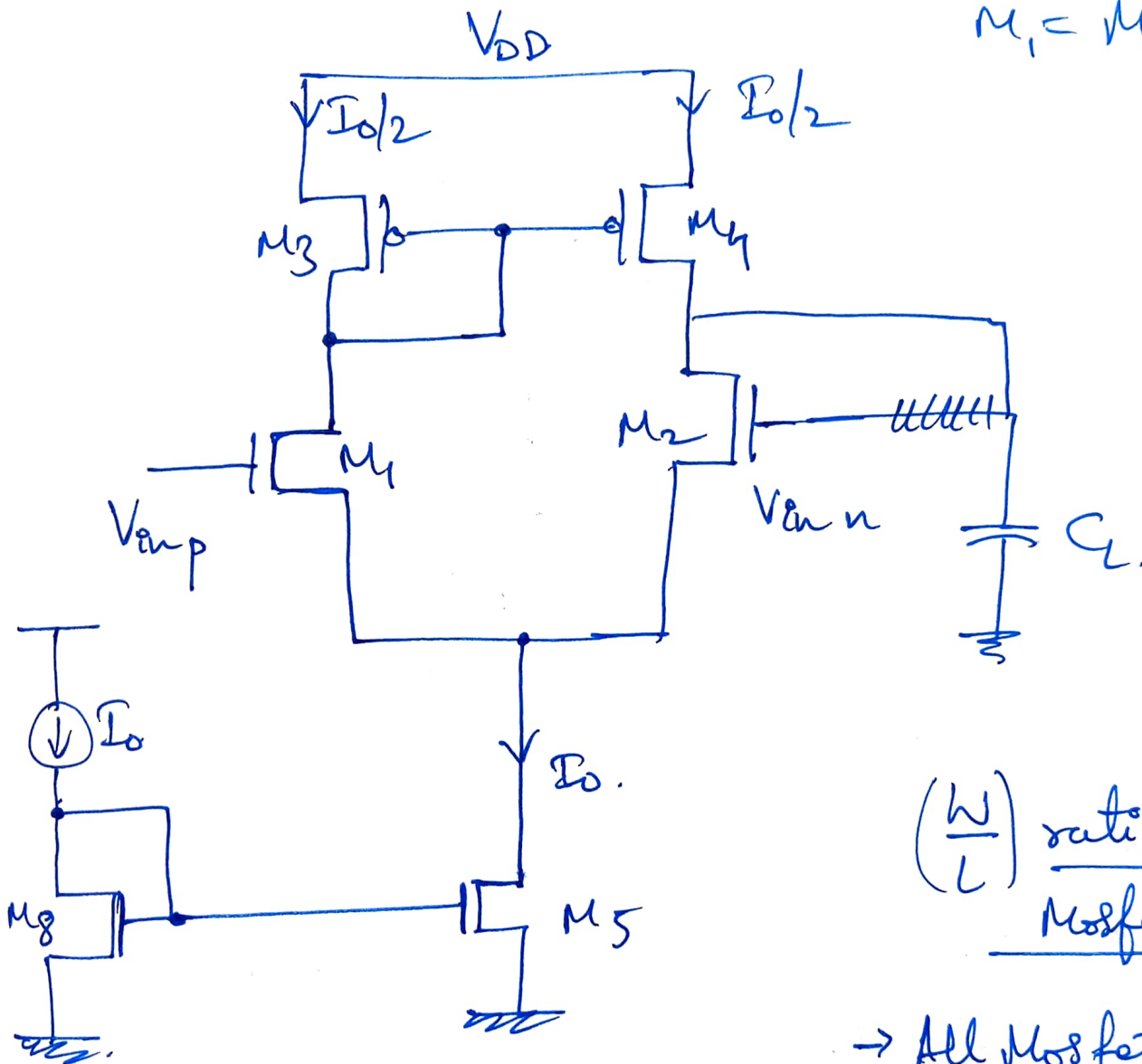
$$\begin{matrix} M_3 = M_4 \\ M_1 = M_2 \end{matrix} \left. \begin{matrix} \\ \end{matrix} \right\} \begin{matrix} \text{Symmet} \\ \text{ric} \end{matrix}$$



$\left(\frac{W}{L}\right)$ ratio of all Mosfets

→ All Mosfets in saturation

→ I_o → slew rate

→ m_3, m_4 → $I_{CMR} +$

→ m_1, m_2 → Gain Bandwidth Product

→ m_5 → $I_{CMR} -$






→ m_6 → I_o & m_5

$$\frac{dV}{dt} ; \phi = CV$$

$$I = C \frac{dV}{dt}$$

$$\boxed{\frac{dV}{dt} = \frac{I_o}{C_L} = \text{slew rate}}$$


Design a 2 staged OPAMP

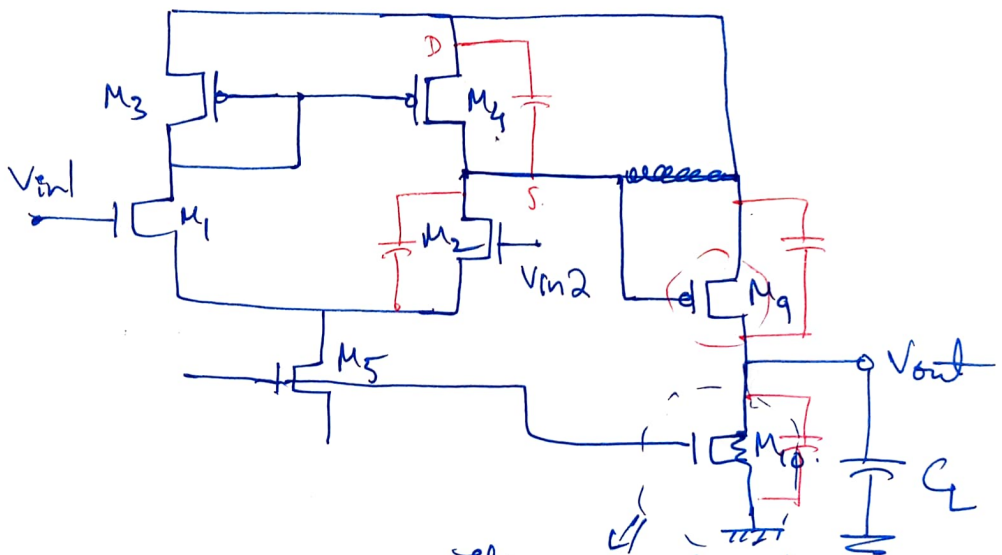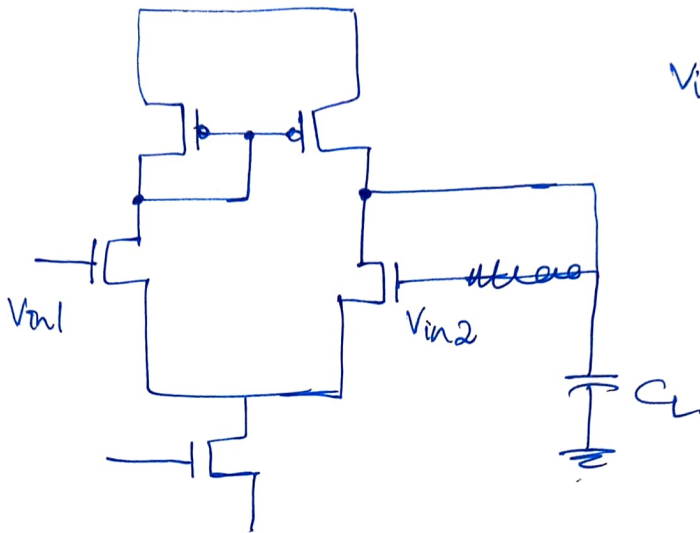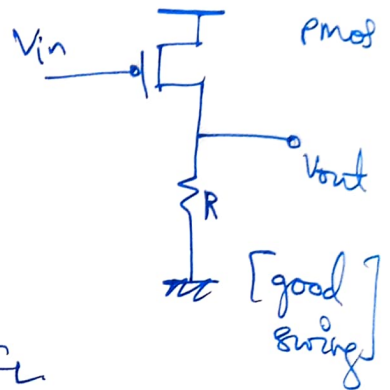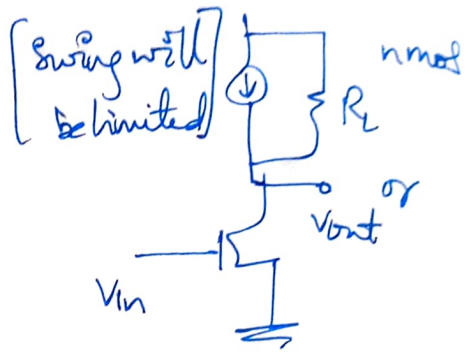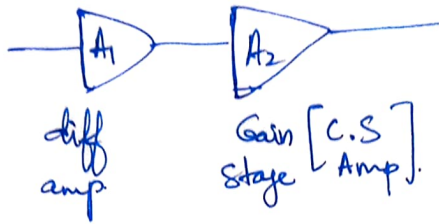


This MOSFET has been used not
- each of Resistors we implemented
a current source using MOSFET

generally each cap of mosfet (D-S) will be present but at 2nd stage ~~at the~~ the load cap will be very large compared to mosfet ones so neglect



Problem 1

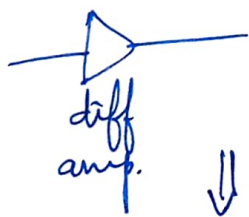

↓ Small Signal

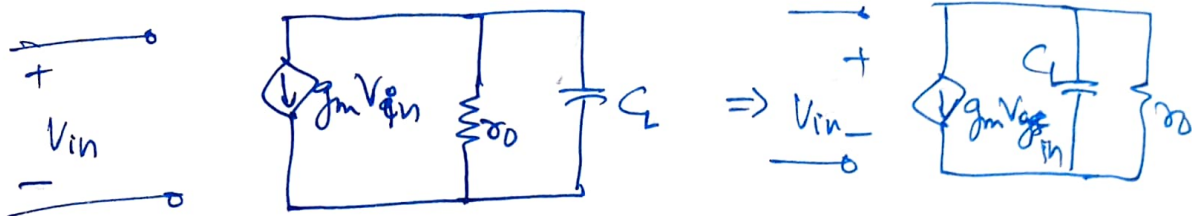

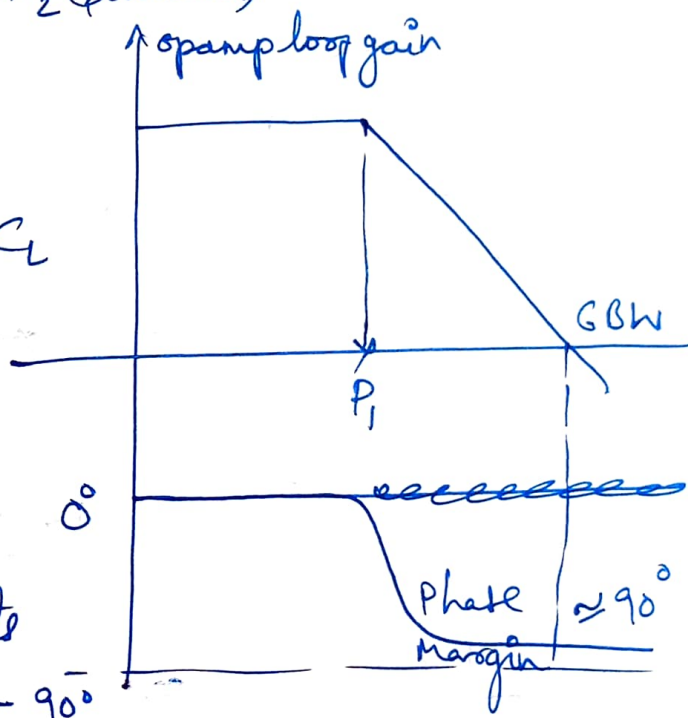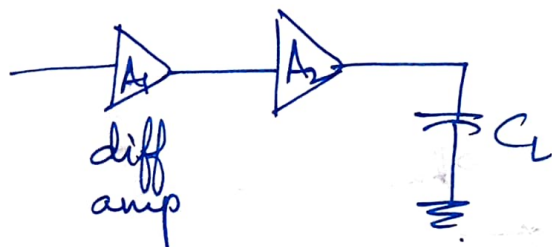
r_{o1} = resistance of M_4 & M_2 (parallel)



C_1 - Capacitance of DS of Mosfet M_4, M_2

$C_2 \approx C_L$

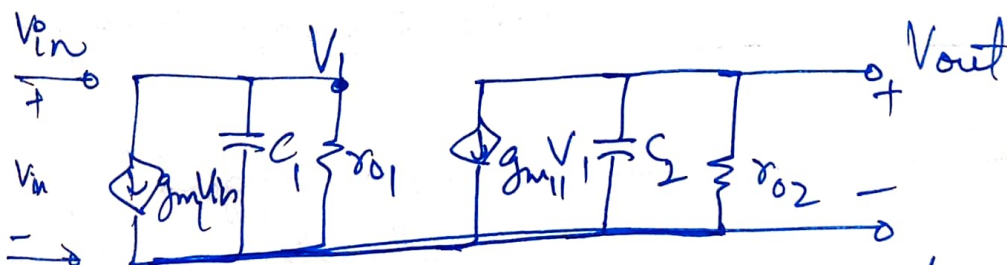
r_{o2} = resistance of Mosfets M_4 parallel to M_{10}



2 port N/w.


$$P_1 = \frac{1}{r_{o1} C_1}$$

$$P_2 = \frac{1}{r_{o2} C_2}$$

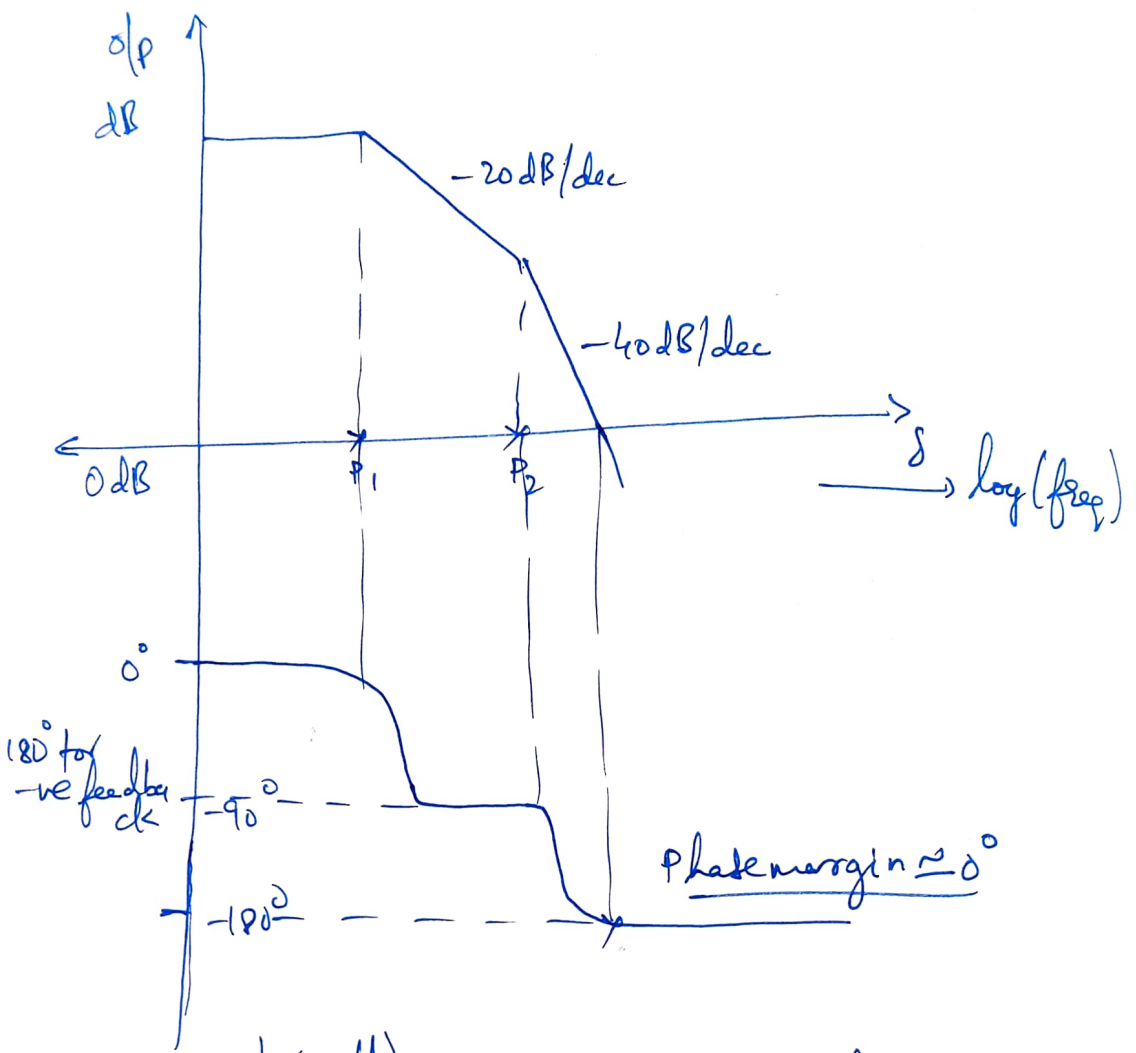

for ult)


for very good phase margin

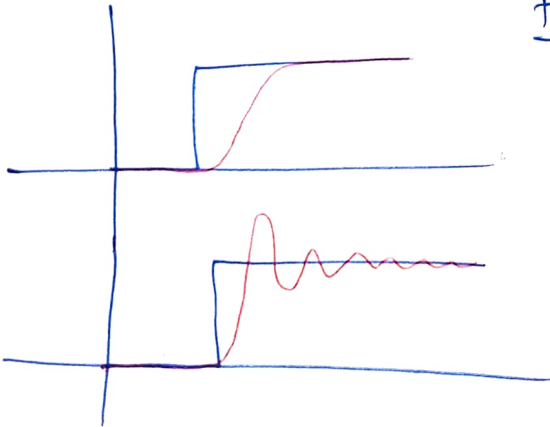

for not good phase margin


$60^\circ \rightarrow$ very good } phase margin
 $45^\circ \rightarrow$ min }

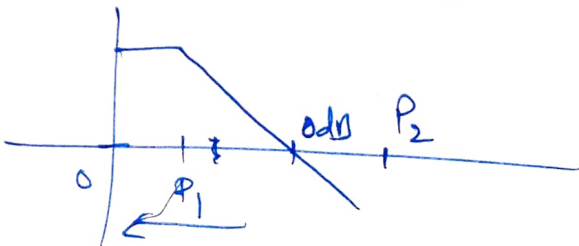$P_1 \rightarrow$ dominant Pole we move it back such that gain crosses 0 dB before P_2



$$P_1 = \frac{1}{r_{o1} C_1} \quad ; \quad P_2 = \frac{1}{r_{o2} C_2}$$

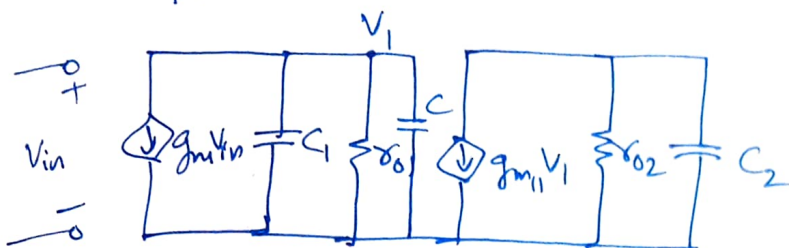
C_1 can be charged
 $C_1 \uparrow \quad P_1 \downarrow$





$$P_1 = \frac{1}{r_{o1} C_1} \sim \frac{1}{r_{o1} (C_1 + C_2)}$$

$C \rightarrow$ should be bigger


To avoid big cap we use Miller effect

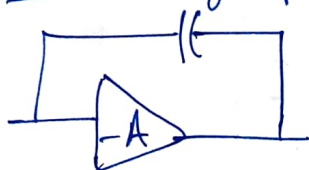


\Rightarrow

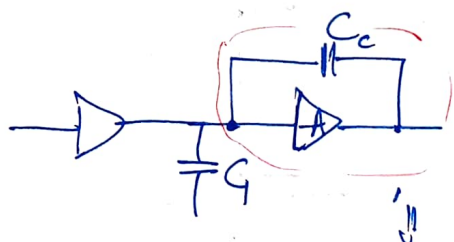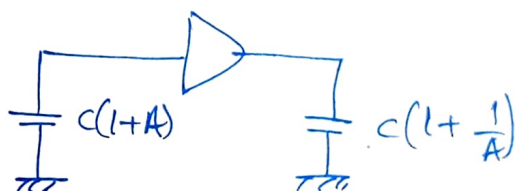

Miller Capacitor!

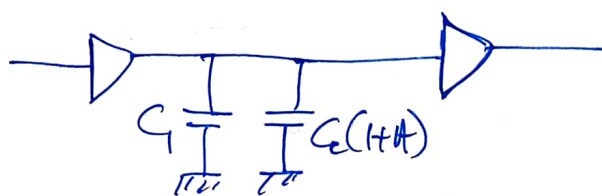

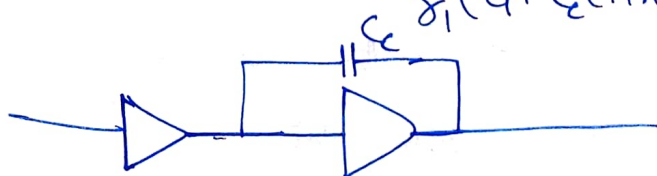
$$P_1 = \frac{1}{r_{o1} (C_1 + C_c (1+A))}$$




Initial $P_1 = \frac{1}{r_{o1} C_1}$

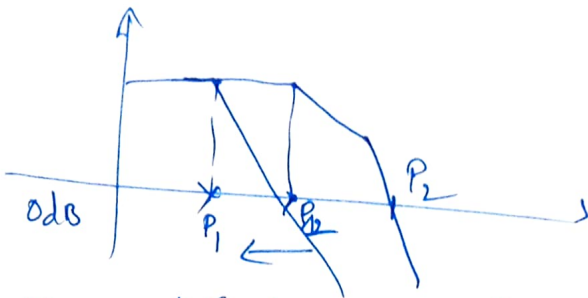
later $P_1 = \frac{1}{r_{o1} [C_1 + C_c (1+A)]}$



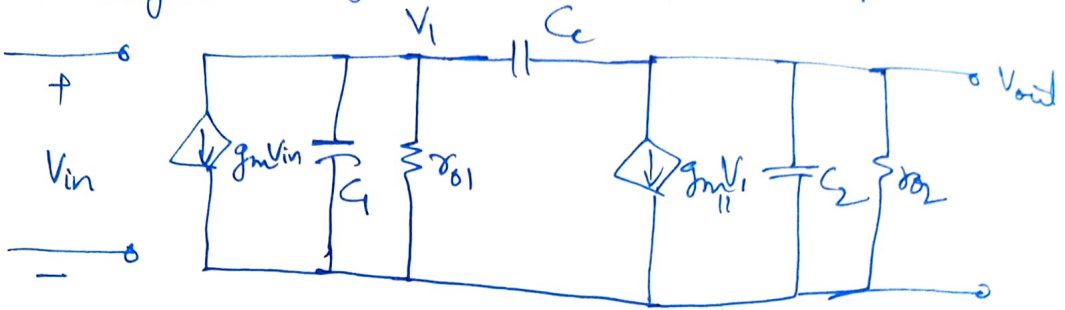Small signal (2 stage OPAMP with compensated cap).



2 stg OPAMP GKT

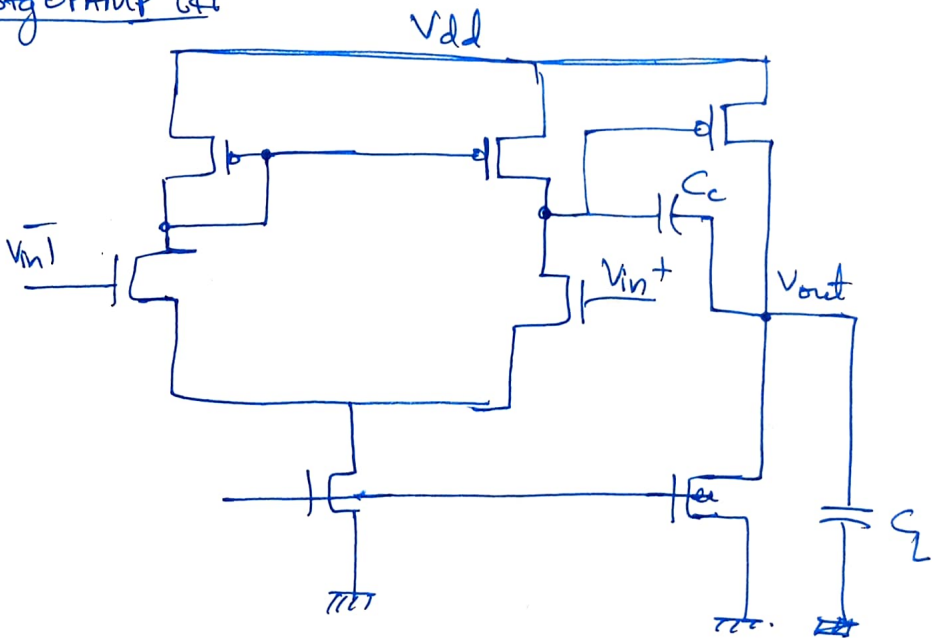


- Phase Margin, -Poles, -Zeros, GBW etc,
- Slew Rate
- Swing Limits

Phase Margin:-


$$\frac{V_o}{V_{in}} =$$

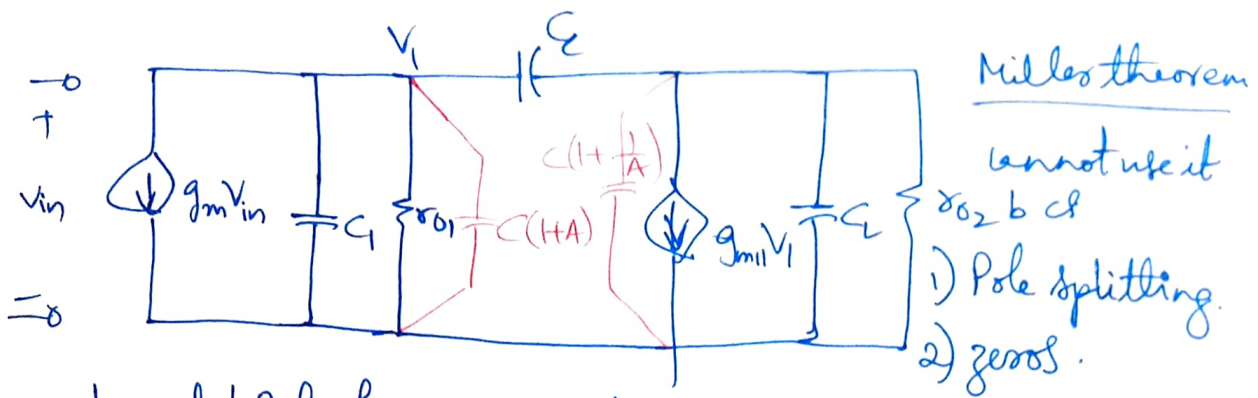from small sig SSA (small signal Analysis)
use Miller theorem which says that C_c can be split into 1 cap at o/p & others at i/p.



because at high freq C acts as a short ckt which cannot be replicated by splitting it.
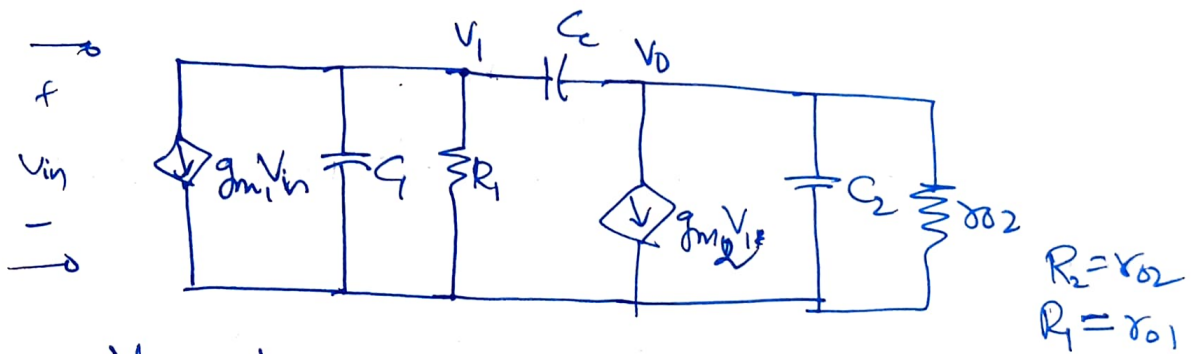
$$\frac{V_1}{V_{in}} \neq \frac{V_o}{V_1} = \frac{V_o}{V_{in}}$$



$$\frac{V_1}{\frac{1}{sC_1}} + \frac{V_1}{R_1} + g_{m1} V_{in} + \frac{V_1 - V_o}{\frac{1}{sC_2}} = 0 \quad \left\{ \text{Nodal eqn} \right.$$

$$V_1 \left(sC_1 + \frac{1}{R_1} + sC_2 \right) + g_{m1} V_{in} - V_o sC_2 = 0$$

$$V_1 = \frac{V_o sC_2 R_1 - g_{m1} V_{in} R_1}{1 + sR_1(C_1 + C_2)} \quad (1)$$

$$\frac{V_o}{\frac{1}{sC_2}} + \frac{V_o}{R_2} + g_{m2} V_1 + \frac{V_o - V_1}{\frac{1}{sC_1}} = 0;$$

$$V_o \left(s(C_2 + C_1) + \frac{1}{R_2} \right) = V_1 \left(sC_2 - g_{m2} \right)$$

$$V_i = \frac{V_o [s(C_2 + C_c) + R_2]}{[sC_c - g_{m2}]}$$


put in (1).

$$V_o \left(s(C_2 + C_c) + \frac{1}{R_2} \right) = \frac{(V_o s C_c R_1 - g_{m1} R_1 V_{in}) (sC_c - g_{m2})}{1 + s(C_1 + C_c) R_1}$$

$$V_o [s(C_2 + C_c) R_2 + 1] [1 + s(C_1 + C_c) R_1] = [V_o \cdot s C_c R_1 - g_{m1} R_1 V_{in}] (sC_c - g_{m2})$$

$$\frac{V_o}{V_{in}} = \frac{g_{m1} R_1 g_{m2} R_2 \left(1 - \frac{sC_c}{g_{m2}} \right)}{s^2 [R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)] + s [R_2 (C_c + C_2) + R_1 (C_c + C_1) + C_c g_{m2} R_1 R_2 + 1]} \quad (2)$$

for simplification

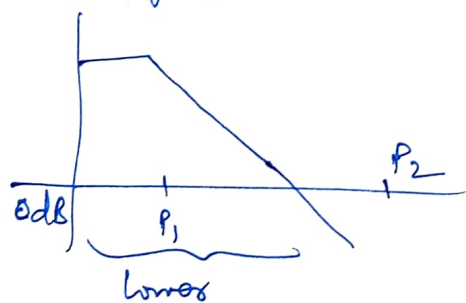

DC $\Rightarrow \omega = s = 0$ [dc gain]

at lower freq

• the coeff of s is dominant


$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{A_{dc} \left(1 - \frac{s}{z} \right)}{\left(1 + \frac{s}{P_1} \right) \left(1 + \frac{s}{P_2} \right)} \\ &= \frac{A_{dc} \left(1 - \frac{s}{z} \right)}{1 + \frac{s^2}{P_1 P_2} + s \left(\frac{1}{P_1} + \frac{1}{P_2} \right)} \quad (3) \end{aligned}$$

Comparing (3) with (2)

we get

$$P_1 P_2 = R_1 R_2 [C_1 C_2 + C_1 C_c + C_2 C_c]$$
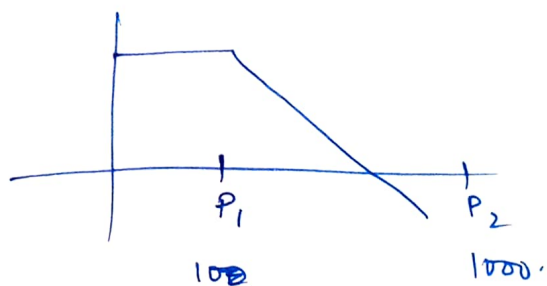
$$\frac{1}{P_1} + \frac{1}{P_2} = R_2 [C_c + C_2] + R_1 [C_c + C_1] + C_c g_{m2} R_1 R_2 + 1$$



$$s\left(\frac{1}{P_1} + \frac{1}{P_2}\right) \approx \frac{s}{P_1}$$

$$\frac{1}{P_1} = \text{coeff of 's'}$$

$$\text{coeff of } s^2 \Rightarrow \frac{1}{P_1 P_2}$$

$g_{m2} R_2 \rightarrow$ gain of one stage

$$P_1 \approx \frac{1}{R_2(C_1 + C_2) + R_1(C_1 + C_2) + \underline{g_{m2} R_2 R_1 C_2}} \quad (\text{dominant / large})$$

$$P_1 \approx \frac{1}{g_{m2} R_2 R_1 C_2} \quad \text{1st pole}$$

$$P_1 P_2 = \frac{1}{R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)}$$

$$P_2 \approx \frac{g_{m2} C_c}{C_1 C_2 + C_1 C_c + \underline{C_2 C_c}}$$

$$P_2 \approx \frac{g_{m2} C_c}{C_2 C_c} \approx \frac{g_{m2}}{C_2}$$

$$P_2 \approx \frac{g_{m2}}{C_2} \quad \text{2nd pole}$$

$$Z = \frac{g_{m2}}{C_c}$$

$$P_1 = \frac{1}{g_{m2} C_c R_1 R_2}$$

$$P_2 = \frac{g_{m2}}{C_2}$$

$$A_{DC} = \left(\frac{V_{out}}{V_{in}} \right)_{s=0}$$

$$A_{DC} = g_{m1} R_1 g_{m2} R_2$$

Gain Band Product (DC Gain $\times P_1$)


$$GBW = \cancel{DC} A_{DC} \times P_1$$

$$= \frac{g_{m1} g_{m2} R_1 R_2 \times 1}{g_{m2} R_1 R_2 C_c} = \frac{g_{m1}}{C_c}$$

$$GBW = \frac{g_{m1}}{C_c}$$


Slew Rate

Single Stage OPAMP:-

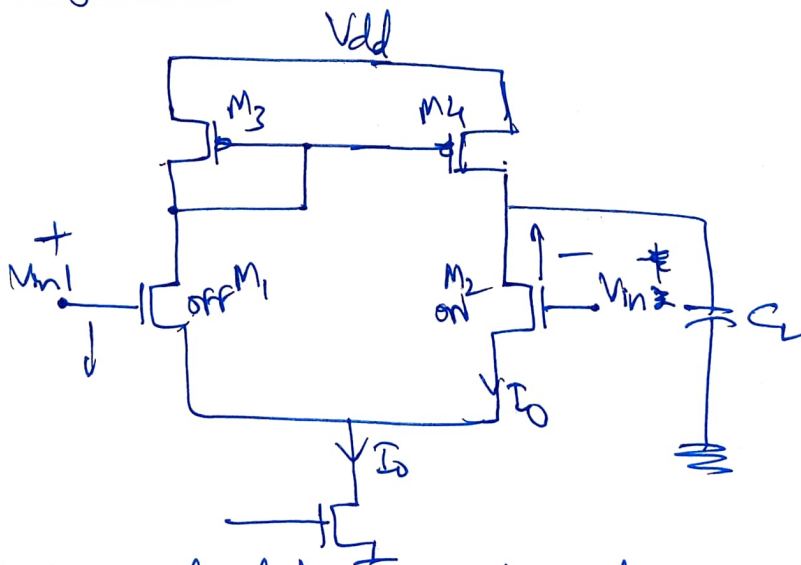

signs are decided + & - bcs at -ve if we increase V_{in} the drain voltage decreases. so it goes into triode region. So when there's a sudden change in i/p, extreme case is M_2 is ON & M_1 is OFF so complete current goes through M_2 . As this is a current mirror no current passes through

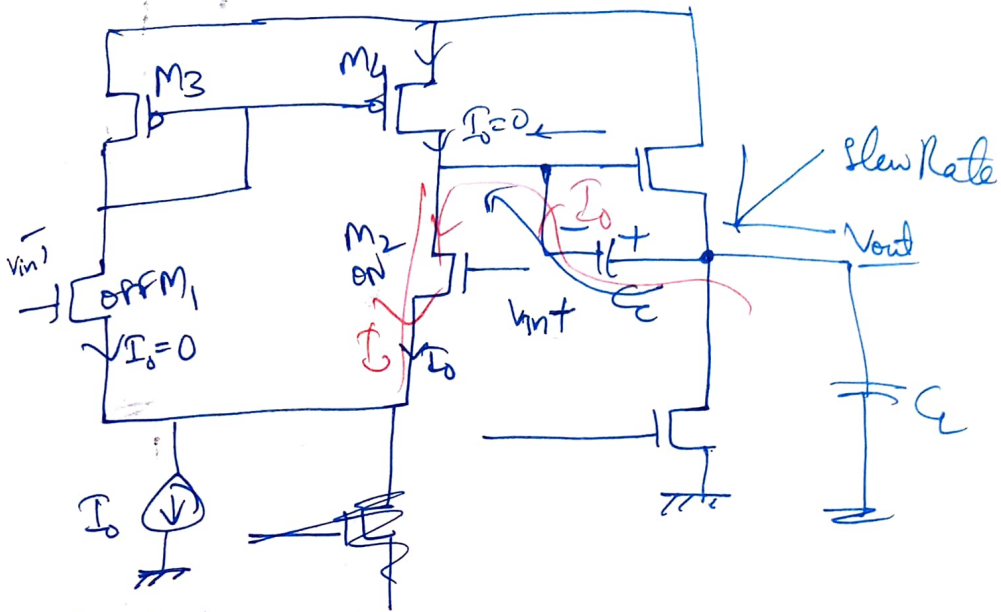$M_3 \& M_4$, so for I_0 to flow it should come from C_p
 so here slew rate was decided by C_c
In 2 stage




Slew Rate

C1 For quick change in I_p for extreme case ~~one is off~~ M_2 is ON. Bcs of current mirror no current will flow across M_1, M_3, M_4 and all current should pass through M_2 should come from C_c

$$\text{So Slew Rate (SR)} = \frac{I_0}{C_c}$$

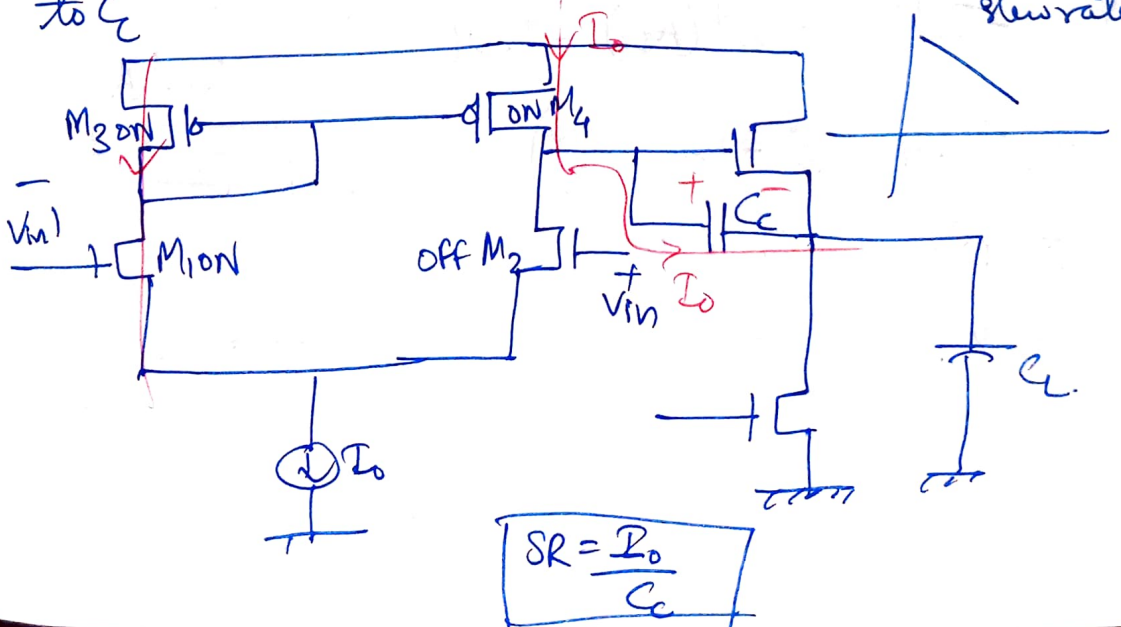C2 Now $M_2 \rightarrow \text{OFF}$, $M_1 \rightarrow \text{ON}$, $M_3, M_4 \rightarrow \text{ON}$, so all current goes to C_c



$$SR = \frac{I_0}{C_c}$$

Phase Margin:

If P_2 moves left the Phase Margin decreases so we're to keep P_2 away from GBW

$$\boxed{Z \geq 10.6B} \quad (1)$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right)$$

$$-\tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right)$$

$$-180^\circ$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right)$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{GBW}{Z}\right) - \tan^{-1}\left(\frac{GBW}{P_1}\right) - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$= -\tan^{-1}\left(\frac{GBW}{10GBW}\right) - \tan^{-1}\left(\frac{g_{m1}/C_c}{g_{m2}R_2C_c}\right)$$

$$- \tan^{-1}\left(\frac{g_{m1}/C_c}{g_{m2}/C_2}\right)$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}(0.1) - \tan^{-1}\left(\frac{g_{m1}g_{m2}R_2C_c}{g_{m2}C_2}\right) - \tan^{-1}\left(\frac{g_{m1}C_2}{g_{m2}C_c}\right)$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}(0.1) - \tan^{-1}(A_{oc}) - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$


$$\tan^{-1}(A_{oc}) \approx 90^\circ$$

$$A_{oc} \gg 1$$

$$-180^\circ + P_m = -5.71 - 90^\circ - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$P_m = 90^\circ - 5.71 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$
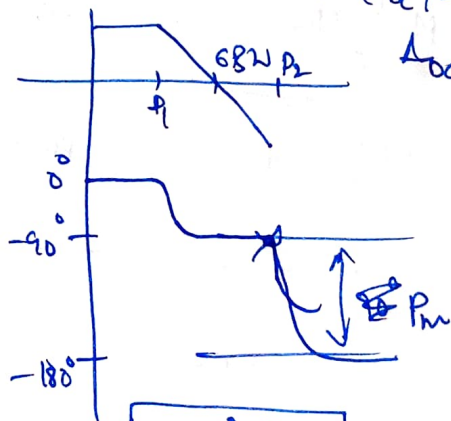
$$P_m = 84.29 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$



$$\boxed{-180^\circ + P_m}$$

for $P_m = 60^\circ$

$$60^\circ = 84.29^\circ - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$\tan^{-1}\left(\frac{GBW}{P_2}\right) = 24.29^\circ$$

$$\frac{GBW}{P_2} = 0.4513$$

$$\boxed{P_2 = \frac{GBW}{0.4513}} \Rightarrow \boxed{P_2 \geq 2.2 GBW} \text{ for } PM = 60^\circ$$

for $P_m = 45^\circ$

$$45^\circ = 84.29^\circ - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$\boxed{P_2 \geq 1.22 GBW} \text{ for } PM = 45^\circ$$

$$P_2 = \frac{g_{m2}}{C_2} \geq 2.22 \frac{g_{m1}}{C_c} \quad \text{as } C_2 \approx C_c$$

$$\Rightarrow \frac{g_{m2}}{C_c} \geq 2.22 \frac{g_{m1}}{C_c}$$

$$\Rightarrow \frac{10}{C_c} > \frac{2.2}{C_c}$$

$$\Rightarrow \boxed{C_c \geq 0.22 C_L}$$

also $Z = 10 GBW$

$$\frac{g_{m2}}{C_c} = 10 \frac{g_{m1}}{C_c}$$

$$\boxed{\frac{g_{m2}}{g_{m1}} = 10}$$

$$\boxed{g_{m2} = 10 g_{m1}}$$